
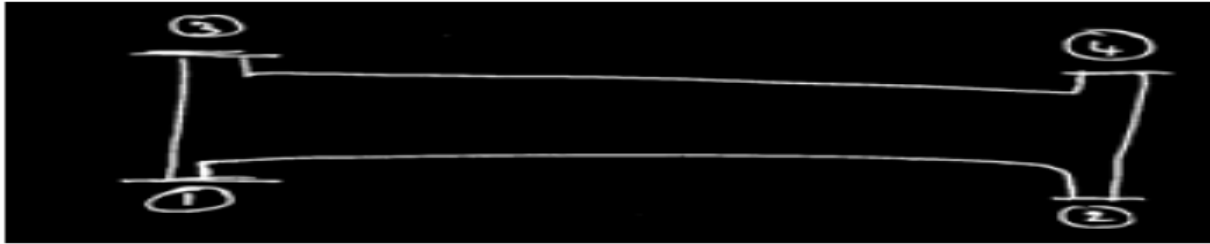


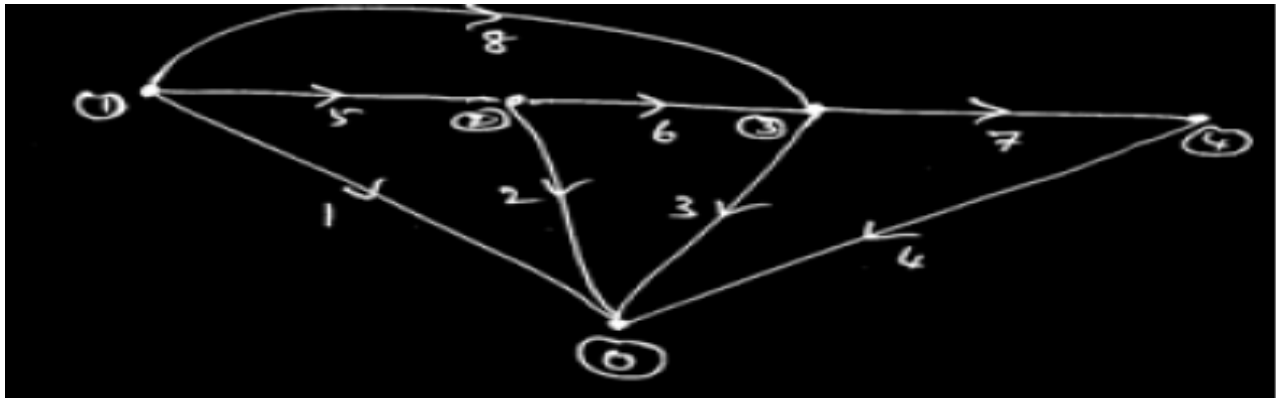
- 1) Determine the incidence matrices  $A$ ,  $B$ ,  $B'$ ,  $C$ ,  $C'$  and  $K$ . From that verify the following relations for the following figure, take 1 as ground bus



- 2) For the figure shown below, the impedance data is given in Table.1. Determine  $Y_{Bus}$  matrix by singular transformation method



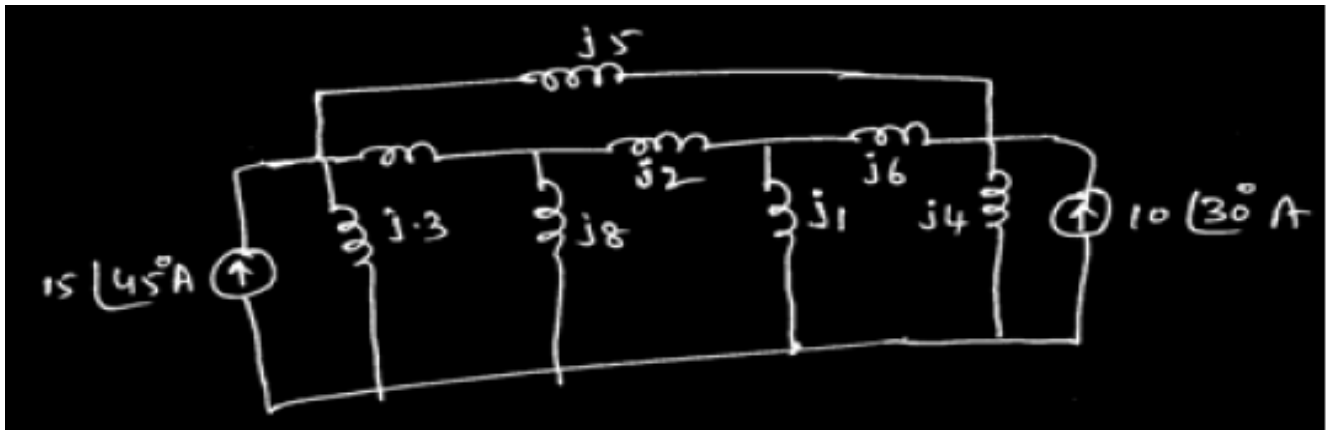- 3) (a) Prove the following relation with one example  $A_b K_T = U$   
 (b) For the network shown in below figure, draw the graph and tree. Also determine the  $Y_{Bus}$  matrix by direct inspection method. All the mentioned values are impedance in p.u



- 4) (a) Define the following  
 (i) Tree (ii) cut set (iii) Tie set  
 (b) Bus incidence matrix is given below, draw the graph and tree

$$A = \begin{array}{c} 1 \\ 2 \\ 3 \\ 4 \end{array} \begin{array}{ccc} \textcircled{1} & \textcircled{2} & \textcircled{3} \\ \left[ \begin{array}{ccc} -1 & 0 & 0 \\ 1 & 0 & -1 \\ 1 & -1 & 0 \\ 0 & -1 & 1 \end{array} \right] \end{array}$$