

Code No: R22043

R10**SET - 1**

II B. Tech II Semester, Supplementary Examinations, Dec – 2012
ELECTRONIC CIRCUIT ANALYSIS
 (Com. to ECE, EIE)

Time: 3 hours

Max. Marks: 75

Answer any **FIVE** Questions
 All Questions carry **Equal** Marks

1. a) Derive the equations for voltage gain, current gain, input impedance and output admittance for a BJT-CC amplifier using low frequency h-parameter model.
 b) Draw the small signal equivalent circuit of FET-CS amplifier and derive the expression for voltage gain. (8M+7M)
2. a) Calculate the Voltage gain, Input Impedance and Output Impedance of a Voltage Series Feedback amplifier having an Open-loop gain $A=300$, $R_i=1.5K\Omega$, $R_o=50K\Omega$ and $\beta= -1/20$.
 b) Explain the general characteristics of negative feedback amplifiers. (7M+8M)
3. a) Perform the generalized analysis of LC oscillators with suitable block diagram and obtain the circuit diagrams of Hartley and Colpitts oscillators.
 b) The ac equivalent circuit of a Crystal has the Values: $L=3$ H, $C_s=0.005pF$, $R= 2K\Omega$ and $C_m=10$ pF. Determine the series and parallel resonant frequencies of the Crystal. (8M+7M)
4. a) Perform the analysis of two stage RC Coupled JFET-CS Amplifier circuit.
 b) Draw the circuit diagram for differential amplifier and perform the analysis with its equivalent circuit. (8M+7M)
5. a) Discuss about Hybrid- π capacitances. How do Hybrid- π parameters vary with temperature?
 b) Following measurements of a certain transistor are available at room temperature and with $I_C = 5$ mA, $h_{fe} = 100$, $h_{ie} = 0.62$ K Ω . Short circuit current gain = $A_{IS} = 10$ at 10MHz. $C_{b'c} = 3pF$. Calculate f_T and f_{β} . (8M+7M)
6. a) Ideal class-B transformer-coupled audio amplifier is fed from 20V DC. Transformer ratio is $\frac{N_p}{N_s} = 4$. A 4 ohm speaker is connected to load. Calculate:
 i) Maximum signal power delivered to load. ii) Power dissipation rating to each transistor.
 iii) Maximum excitation current at input if transfer characteristic is linear ($h_{fe} = 20$).
 b) Show that class B push pull amplifiers exhibit half wave symmetry. (7M+8M)
7. a) Derive the expression for the gain of a single-tuned capacitance coupled amplifier. Discuss about its Selectivity.
 b) Draw and explain the circuit diagram for single tuned capacitive coupled amplifier and derive the expression for (A/A_{reso}) . (8M+7M)
8. a) Draw the circuit and explain how short circuit over load protection is provided in Voltage Regulators circuits.
 b) Design a zener-shunt regulator with the specifications using a zener diode with $V_Z = 10V$. Input supply voltage varies from 15V to 25V and the load current varies between 0 and 15 mA. Also determine the line and load regulation. (8M+7M)

Code No: R22043

R10**SET - 2**

II B. Tech II Semester, Supplementary Examinations, Dec – 2012
ELECTRONIC CIRCUIT ANALYSIS
 (Com. to ECE, EIE)

Time: 3 hours

Max. Marks: 75

Answer any **FIVE** Questions
 All Questions carry **Equal** Marks

- ~~~~~
1. a) Perform the generalized analysis of single stage BJT-CE amplifier using h-parameter model.
 b) Draw the Small Signal model of JFET-CS amplifier and derive the expressions for the voltage gain, the output impedance and the input impedance. (8M+7M)

 2. a) What are the different types of negative feedback? Explain how the input and output impedances of an amplifier are affected by the different types of negative feedback.
 b) The open loop voltage gain of the amplifier of an amplifier is 50. Its input impedance is 1k Ω . What will be the input impedance where a negative feedback of 10% is applied to the amplifier? (10M+5M)

 3. a) Draw the circuit of Hartley oscillator and explain its working. Derive the expressions for frequency of oscillation and condition for starting of oscillation.
 b) Draw the equivalent circuit of a quartz crystal. What makes the quartz produce stable oscillations? (10M+5M)

 4. a) Draw the circuit diagram of cascode-transistor amplifier Circuit and analyze its performance.
 b) Draw and explain the working of two-stage BJT-RC Coupled amplifier. Derive the expression for its voltage gain. (7M+8M)

 5. a) Explain the concept of CE short circuit current gain with its equivalent circuit. Derive the necessary expressions.
 b) The following low-frequency parameters are available for a transistor at

$I_{CQ} = 5 \text{ mA}$		
$h_{ie} = 1\text{K}$,	$h_{fe} = 100$	$h_{oe} = 4 \times 10^{-5} \text{ A/V}$
$h_{re} = 10^{-4}$	$C_{ob} = 2 \text{ pF}$	$f_T = 10 \text{ MHz}$

 Compute the values of hybrid- π parameters at room temperature. (8M+7M)

