

Code No: ZO422/R07

Set No. 1

I B.Tech Supplementary Examinations, January 2014
NETWORK ANALYSIS
 (Common to ECE,EIE,BME,E.Con.E,ETE and ECC)

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
 All Questions carry equal marks

1. For the circuit shown in figure 1 find the current I using Kirchoff's laws. [16]

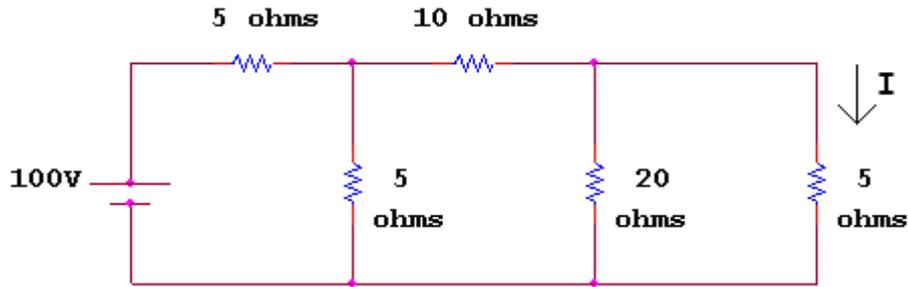


Figure 1

2. Write short notes on [4×4]

- (a) Flux linkage
- (b) Self-induction
- (c) Mutual inductance
- (d) Lenz's law.

3. A 3 phase, 400 V supply is given to a balanced star connected load of impedance $8 + j6$ ohms in each branch. Find the line current, power factor and total power. [16]

4. In the network shown in figure 4 the numerical values of resistances also indicate the branch numbers. Write the oriented graph of the network. Select a tree with branches 1, 2, 3 as the tree branches, write tie-set and cut-set schedule. [16]

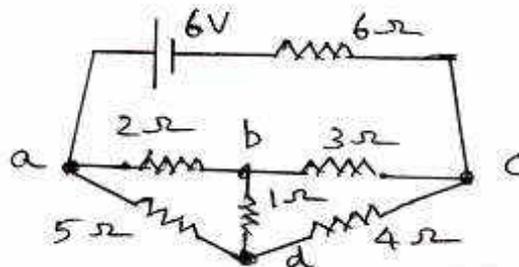


Figure 4

5. (a) State and explain Thevenin's Theorem.



Code No: ZO422/R07

Set No. 1

- (b) What are the limitations of Thevenin's Theorem.
- (c) Explain the steps to apply Thevenin's Theorem and draw the Thevenin's equivalent circuit. [6+4+6]
6. For the bridged T-network shown in the figure 6. Find the driving point admittance Y_{11} and transfer admittance Y_{21} with 2Ω load resistor connected across port - 2. [16]

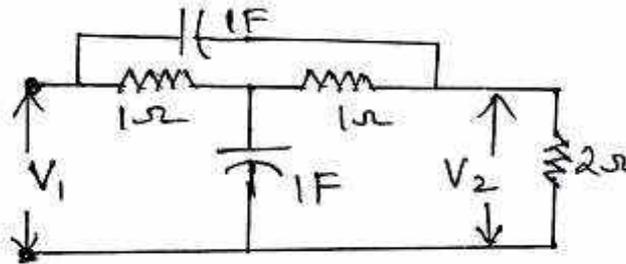


Figure 6

7. In the circuit shown in figure 7, $E_g(t) = 2.5 t$ Volts. What are the values of $i(t)$ and $V_L(t)$ at $t = 4$ seconds. [16]

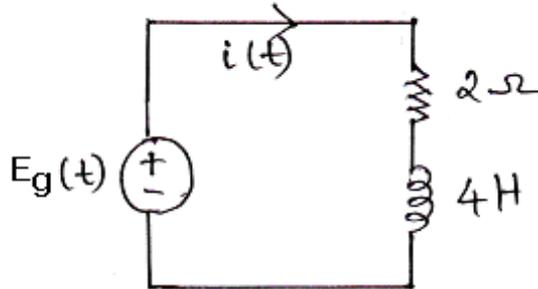


Figure 7

8. Design a BPF with characteristic impedance 100 ohm and a pass band from 48000 Hz and 5200 Hz. [16]



Code No: ZO422/R07

Set No. 2

I B.Tech Supplementary Examinations, January 2014
NETWORK ANALYSIS
 (Common to ECE,EIE,BME,E.Con.E,ETE and ECC)

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

1. For the circuit shown in figure 1, find the current in each branch. [16]

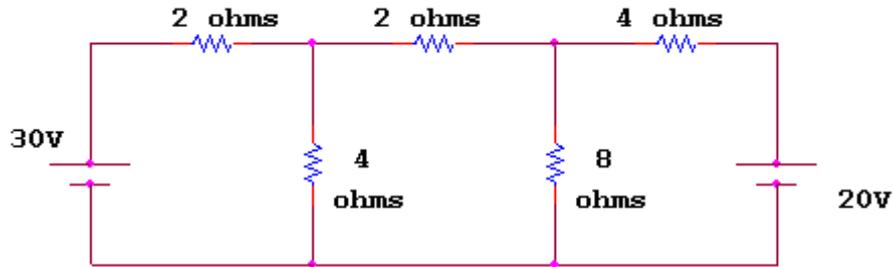


Figure 1

2. Derive expression for R.M.S. and average value of a sinusoidal alternating quantity. [16]
3. A RLC series circuit with a resistance of 10Ω , impedance of $0.2H$ and a capacitance of $40\mu F$ is supplied with a $100V$ supply at variable frequency. Find the following w.r.t. the series resonant circuit. [16]
- (a) the frequency at resonance
 - (b) the current
 - (c) Power
 - (d) Power factor
 - (e) voltage across R, L and C at that time
 - (f) quality factor of the circuit
 - (g) half power points
 - (h) phasor diagram.
4. For the graph in the figure 4, write the cut set schedule and obtain the relation between tree branch voltages and branch voltages. [16]

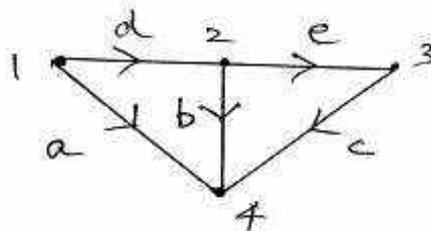


Figure 4



Code No: ZO422/R07

Set No. 2

5. (a) State and explain Thevenin's Theorem.
 (b) What are the limitations of Thevenin's Theorem.
 (c) Explain the steps to apply Thevenin's Theorem and draw the Thevenin's equivalent circuit. [6+4+6]

6. Two identical sections of the network shown in figure 6 are connected in parallel. Obtain the Y parameters of the resulting n/w and verify the result by direct calculation. [16]

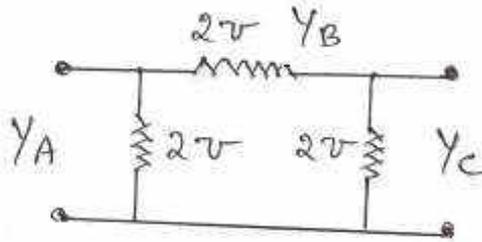


Figure 6

7. Derive the transient response of RLC series circuit with unit step input. [16]

8. Design a composite low pass filter to meet the following specifications. The filter is to be terminated in 500 ohms resistance and it is to have a cutoff of 1000 Hz with very high attenuation at 1065 and 1250 Hz. [16]

Code No: ZO422/R07

Set No. 3

**I B.Tech Supplementary Examinations, January 2014
NETWORK ANALYSIS**

(Common to ECE,EIE,BME,E.Con.E,ETE and ECC)

Time: 3 hours

Max Marks: 80

**Answer any FIVE Questions
All Questions carry equal marks**

1. In the circuit as shown in figure 1 find the currents in all the resistors. Also calculate the supply voltage & power supplied by the source. [16]

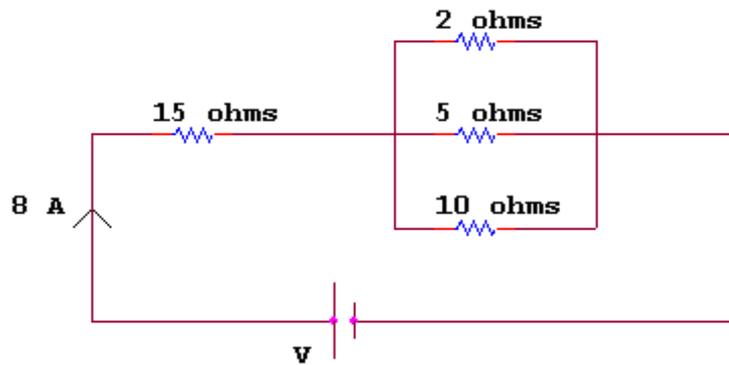


Figure 1

2. A series circuit consists of R and L and is supplied by a sinusoidal ac voltage source. Derive expressions for
- (a) impedance,
 - (b) current,
 - (c) power factor. Draw the vector diagram. [16]
3. An inductive coil of Resistance R and inductance L is connected in parallel with a capacitor C. Derive the expressions for resonant frequency and Q factor. [16]
4. Write the node voltage equations and determine the currents in each branch for the network shown in figure 4. [16]

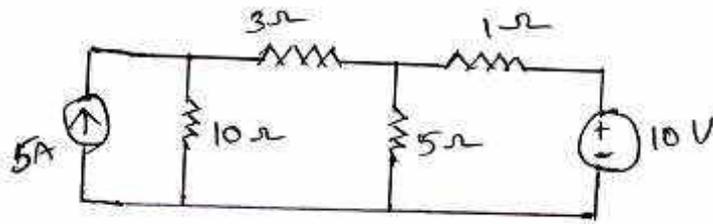


Figure 4

5. Find the Norton's equivalent across the terminals ab as shown in the figure 5. Hence find current through 10 ohms. [16]



Code No: ZO422/R07

Set No. 3

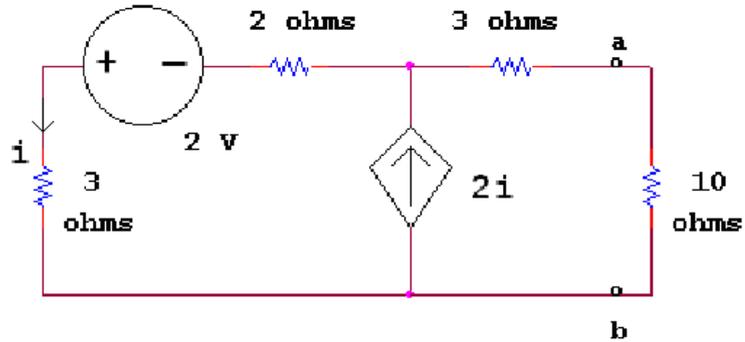


Figure 5

6. For the bridged T-network shown in the figure 6. Find the driving point admittance Y_{11} and transfer admittance Y_{21} with 2Ω load resistor connected across port - 2. [16]

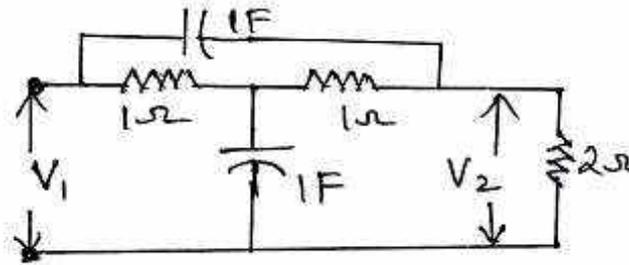


Figure 6

7. Derive the transient response of RLC series circuit with unit step input. [16]
8. Design a composite low pass filter to meet the following specifications. The filter is to be terminated in 500 ohms resistance and it is to have a cutoff of 1000 Hz with very high attenuation at 1065 and 1250 Hz. [16]



Code No: ZO422/R07

Set No. 4

I B.Tech Supplementary Examinations, January 2014
NETWORK ANALYSIS
 (Common to ECE,EIE,BME,E.Con.E,ETE and ECC)

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
 All Questions carry equal marks

1. Using star delta conversion find the current I in the circuit as shown in figure 1. [16]

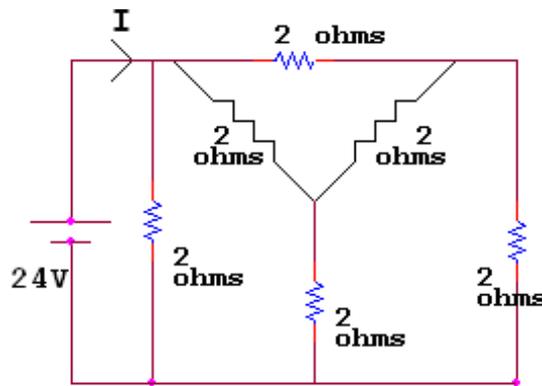


Figure 1

2. A series circuit consists of R and L and is supplied by a sinusoidal ac voltage source. Derive expressions for
- (a) impedance,
 - (b) current,
 - (c) power factor. Draw the vector diagram. [16]
3. Show that the resonant frequency of a series RLC circuit is $f_r = 1 / (2\pi \sqrt{LC})$. Also derive the expressions for Q factor. [16]
4. For the network shown in figure 4 draw oriented graph and draw all possible trees. [16]

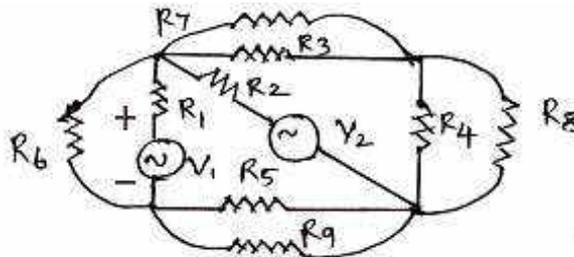


Figure 4

5. (a) State and explain Thevenin's Theorem.
 (b) What are the limitations of Thevenin's Theorem.



Code No: ZO422/R07

Set No. 4

(c) Explain the steps to apply Thevenin's Theorem and draw the Thevenin's equivalent circuit. [6+4+6]

6. For the two port network shown in the figure 6, the currents I_1 and I_2 entering at port 1 and 2 respectively are given by the equations.

$$I_1 = 0.5 V_1 - 0.2 V_2$$

$$I_2 = -0.2V_1 + V_2$$

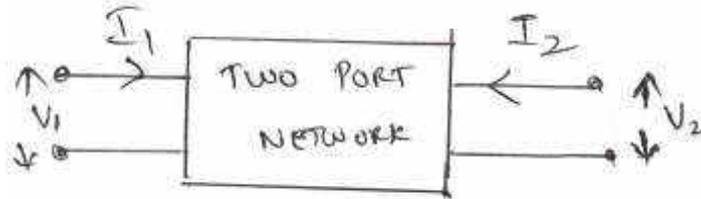


Figure 6

Where V_1 and V_2 are the port voltages at port 1 and 2 respectively. Find the Y, Z, ABCD parameters for the network. Also find its equivalent Π network. [16]

7. In the circuit shown in figure 7, $E_g(t) = 2.5 t$ Volts. What are the values of $i(t)$ and $V_L(t)$ at $t = 4$ seconds. [16]

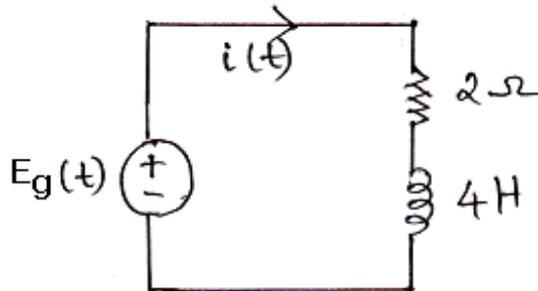


Figure 7

8. Obtain the constant low pass filter and high pass filter characteristics for the circuit, as shown in figure 8. [16]

$$R = 1000\Omega$$

$$C = 10 \mu F$$

$$F = 1 \text{ KHz}$$

$$Q = 5.$$

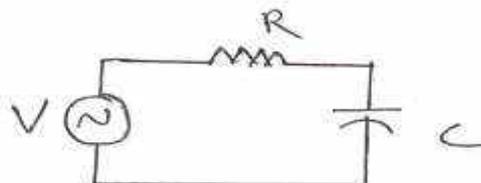


Figure 8

